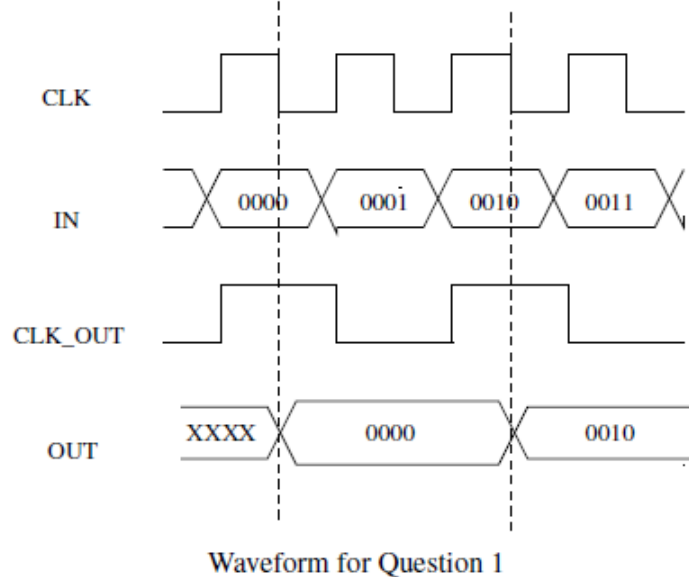


Khanh Nguyen
UIN 525000335
ECEN 449-503
Dr.Khatri

Homework 1

1. [10 points.]

Consider an input clock signal CLK which operates at 20 MHz. Also consider a signal IN which is 4 bits wide, arriving at every positive edge of CLK. Write Verilog code whose output is the signal OUT shown below. Write a testbench to simulate your code. Test your code for 16 clock cycles, with the input IN = 0000 for the first clock cycle, 0001 for the second cycle, and so on.



Answer:

Verilog code:

```
`timescale 1ns / 1ps
`default_nettype none

module hw1_q1(CLK, IN, CLK_OUT, OUT);
    input wire CLK;
    input wire [3:0] IN;
    output reg [3:0] OUT;
    output reg [3:0] CLK_OUT;

    initial CLK_OUT = 0;
    initial OUT = 4'b0000;
```

```

always@(posedge CLK)//CLK_OUT changes at pos edge
begin
    CLK_OUT = ~CLK_OUT;
end

always@(CLK_OUT)//OUT changes at CLK_OUT
begin
    OUT= IN;
end

endmodule // hw1_q1

```

Test bench:

```

`timescale 1ns / 1ps
`default_nettype none
module hw1_q1_tb;
    //Inputs
    reg CLK;
    reg [3:0] IN;
    //Outputs
    wire [3:0] OUT;
    wire CLK_OUT;

    //Instantiate the Unit Under Test (UUT)
    hw1_q1 uut(
        .CLK(CLK),
        .IN(IN),
        .CLK_OUT(CLK_OUT),
        .OUT(OUT)
    );

    //generate 20MHz clock signal
    always
        #25 CLK = ~CLK; //since 2MHz is 50ns per cycle
                                //=>#25 half cycle

    initial begin
        CLK=0;
        #25 IN=4'b0000; //inputs
        #25 IN=4'b0001;
    end
endmodule

```

```


#25 IN=4'b0010;
#25 IN=4'b0011;
#25 IN=4'b0100;
#25 IN=4'b0101;
#25 IN=4'b0110;
#25 IN=4'b0111;
#25 IN=4'b1000;
#25 IN=4'b1001;
#25 IN=4'b1010;
#25 IN=4'b1011;
#25 IN=4'b1100;
#25 IN=4'b1101;
#25 IN=4'b1110;
#25 IN=4'b1111;

end

endmodule // hw1_q1_tb

```

Result:

 

Result waveform

2. [10 points.]

Write a C program that reads a character string from an input file and arranges the words in that string lexicographically (as shown below) and writes the result to an output file. The input file name is IN.txt and the output file name is OUT.txt. Both these files contain exactly one line. For example if the input file contains

This is an example string.

then output file should contain

an example is string. This

Test your code on the following strings

- (a) Hello hola how are you
- (b) The big cat ate the apple

Answer:

C code:

```
#include <stdio.h>
#include <string.h>
#include <stdlib.h>

void sort(char arr[][100], int n)
{
    int i, j, min_idx;
    // One by one move boundary of unsorted subarray
    char minStr[100];
    for (i = 0; i < n-1; i++)
    {
        // Find the minimum element in unsorted array
        int min_idx = i;
        strcpy(minStr, arr[i]);
        for (j = i+1; j < n; j++)
        {
            // If min is greater than arr[j]
            if (strcmp(minStr, arr[j]) > 0)
            {
                // Make arr[j] as minStr and update min_idx
                strcpy(minStr, arr[j]);
                min_idx = j;
            }
        }
        // Swap the found minimum element with the first element
        if (min_idx != i)
        {
```

```

        char temp[100];
        strcpy(temp, arr[i]); //swap item[pos] and item[i]
        strcpy(arr[i], arr[min_idx]);
        strcpy(arr[min_idx], temp);
    }
}

int main(){
char words[100][100]; // to save words
int i=0;
int j=0;

printf("\nInput read from Input2.txt is:\n");
// Reads input file
FILE *fptr;
fptr = fopen("Input2.txt", "r");
while(!feof(fptr)){
    fscanf(fptr,"%s",&words[i]); // read from file
    printf("%s ",words[i]); // print to screen
    i++;
}
fclose(fptr); // close file
printf("\n\n");
sort(words,i); // sort the array
printf("Check the file Output2.txt for result. \n\n");
printf("This is the output: \n");

//Writes output on screen and to file
FILE *output;
output = fopen("Output2.txt", "w");
for(j=0 ; j<i; j++){
    printf("%s ",words[j]); // print to screen
    fprintf(output,"%s",&words[j]); // print into file
}
fclose(output); // close file
printf("\n");
return 0;
}

```

Results:

Sentence 1:

```
[k41nt]@hera3 ~/ECEN449/Hw1/Q2> (22:56:40 02/14/18)
:: gcc -o out hw1_q2.c

[k41nt]@hera3 ~/ECEN449/Hw1/Q2> (22:57:16 02/14/18)
:: ./out

Input read from Input1.txt is:
Hello hola how are you

Check the file Output1.txt for result.

This is the output:
are Hello hola how you
```

Sentence 2:

```
[k41nt]@hera3 ~/ECEN449/Hw1/Q2> (22:57:17 02/14/18)
:: gcc -o out hw1_q2.c

[k41nt]@hera3 ~/ECEN449/Hw1/Q2> (22:58:21 02/14/18)
:: ./out

Input read from Input2.txt is:
The big cat ate the apple

Check the file Output2.txt for result.

This is the output:
apple ate big cat the The
```

3. [10 points.]

Design an 8-function ALU that accepts 4-bit inputs a and b , a 3-bit input signal $select$, and produces a 5-bit output out . The ALU implements the following functions based on 3-bit input signal $select$.

 $select$ signal function

3'b000 out = a
3'b001 out = $a+b$
3'b010 out = $a-b$
3'b011 out = a/b
3'b100 out = $a\%b$ (remainder)
3'b101 out = $a << 1$
3'b110 out = $(a \geq b)$ (magnitude comparison)
3'b111 out = $(a > b)$ (magnitude comparison)

You must simulate all these eight functions using a testbench. For each of these functions, test the design for 9 values in all ($a = 3, 2, 1$ and $b = 1, 2, 3$.)

Answer:

Verilog code:

```
`timescale 1ns / 1ps
`default_nettype none

module ALU(OUT, A, B, SEL);
input [3:0] A;
input [3:0] B;
output [4:0] OUT;
input [2:0] SEL; //SELECT signal
reg [4:0] OUT;

// Arithmetic operations based on SELECT signal
always@(A or B or SEL)
begin
    case(SEL)
        3'b000:
            OUT = A;
        3'b001:
            OUT = A+B;
        3'b010:
            OUT = A-B;
        3'b011:
            OUT = A/B;
        3'b100:
            OUT = A%B;
    endcase
end
```

```

        3'b101:
            OUT = A<<1;
        3'b110:
            OUT = A>=B;
        3'b111:
            OUT = (A>B);
    default:
        OUT = 5'b111111;
    endcase
end
endmodule

```

Test bench:

```

`timescale 1ns / 1ps
`default_nettype none

module ALU_TEST;
wire [4:0] out;
reg [3:0] a;
reg [3:0] b;
reg [2:0] select;

ALU ALU_test(out,a,b,select);

    initial
        begin
            $monitor($time, " Sel=%b ,A=%d ,B=%d ,Out=%d", select, a, b, out);
            select = 3'b000; a=4'b0000; b=4'b0000;
            #10 select = 3'b001; a=4'b0011; b=4'b0001;
            #10 select = 3'b010; a=4'b0011; b=4'b0001;
            #10 select = 3'b011; a=4'b0011; b=4'b0001;
            #10 select = 3'b100; a=4'b0011; b=4'b0001;
            #10 select = 3'b101; a=4'b0011; b=4'b0001;
            #10 select = 3'b110; a=4'b0011; b=4'b0001;
            #10 select = 3'b111; a=4'b0011; b=4'b0001;
            #10 select = 3'b000; a=4'b0010; b=4'b0010;
            #10 select = 3'b001; a=4'b0010; b=4'b0010;
            #10 select = 3'b010; a=4'b0010; b=4'b0010;
            #10 select = 3'b011; a=4'b0010; b=4'b0010;
            #10 select = 3'b100; a=4'b0010; b=4'b0010;
            #10 select = 3'b101; a=4'b0010; b=4'b0010;

```



```

#10 select = 3'b110; a=4'b0010; b=4'b0010;
#10 select = 3'b111; a=4'b0010; b=4'b0010;
#10 select = 3'b000; a=4'b0001; b=4'b0011;
#10 select = 3'b001; a=4'b0001; b=4'b0011;
#10 select = 3'b010; a=4'b0001; b=4'b0011;
#10 select = 3'b011; a=4'b0001; b=4'b0011;
#10 select = 3'b100; a=4'b0001; b=4'b0011;
#10 select = 3'b101; a=4'b0001; b=4'b0011;
#10 select = 3'b110; a=4'b0001; b=4'b0011;
#10 select = 3'b111; a=4'b0001; b=4'b0011;
#300 $finish;
end

```

endmodule

Result:

```

# run 1000ns

0 Sel=000 ,A= 0 ,B= 0 ,Out= 0
10 Sel=001 ,A= 3 ,B= 1 ,Out= 4
20 Sel=010 ,A= 3 ,B= 1 ,Out= 2
30 Sel=011 ,A= 3 ,B= 1 ,Out= 3
40 Sel=100 ,A= 3 ,B= 1 ,Out= 0
50 Sel=101 ,A= 3 ,B= 1 ,Out= 6
60 Sel=110 ,A= 3 ,B= 1 ,Out= 1
70 Sel=111 ,A= 3 ,B= 1 ,Out= 1
80 Sel=000 ,A= 2 ,B= 2 ,Out= 2
90 Sel=001 ,A= 2 ,B= 2 ,Out= 4
100 Sel=010 ,A= 2 ,B= 2 ,Out= 0
110 Sel=011 ,A= 2 ,B= 2 ,Out= 1
120 Sel=100 ,A= 2 ,B= 2 ,Out= 0
130 Sel=101 ,A= 2 ,B= 2 ,Out= 4
140 Sel=110 ,A= 2 ,B= 2 ,Out= 1
150 Sel=111 ,A= 2 ,B= 2 ,Out= 0
160 Sel=000 ,A= 1 ,B= 3 ,Out= 1
170 Sel=001 ,A= 1 ,B= 3 ,Out= 4
180 Sel=010 ,A= 1 ,B= 3 ,Out=30
190 Sel=011 ,A= 1 ,B= 3 ,Out= 0
200 Sel=100 ,A= 1 ,B= 3 ,Out= 1
210 Sel=101 ,A= 1 ,B= 3 ,Out= 2
220 Sel=110 ,A= 1 ,B= 3 ,Out= 0
230 Sel=111 ,A= 1 ,B= 3 ,Out= 0

$finish called at time : 530 ns : File "C:/School/Spring 2018/ECEN 449/HW1/Q3/hw1_q3_tb.v" Line 39
INFO: [USF-XSim-96] XSim completed. Design snapshot 'ALU TEST behav' loaded.

```

4. [10 points.]

Consider a 12 bit serial data string DAT, which arrives at 10 Mbps. Write Verilog code to count the number of occurrences of “000” in DAT. Simulate the Verilog code using a testbench, using the following values of DAT:

- (a) 000100111000
(b) 110001101101
(c) 100100100000

Answer:

Verilog code:

```
module occur_counter(in, reset, clk, out, count);  
    input in;  
    input clk;  
    input reset;  
    output reg out;  
    output reg [2:0] count;  
    reg [1:0] stt; //state  
  
    always @(posedge clk or negedge reset)  
        if (reset==1)  
            begin  
                stt=2'b00;  
                out=0;  
                count=0;  
            end  
        else  
            begin  
                case (stt)  
  
                    2'b00: //first state  
                        if (in==0)  
                            begin stt=2'b01;//move to next state  
                                out=0;  
                            end  
                        else  
                            begin stt=2'b00; //otherwise stay  
                                out=0;  
                            end  
  
                    2'b01: //second state  
                        if (in==0)  
                            begin stt=2'b10; //move to next state  
                                out=0;
```

```

                                end
                            else
                                begin stt=2'b00; //otherwise stay
                                    out=0;
                                end

                                2'b10: // third state
                                if (in==0)
                                    begin stt=2'b10; // third 0 caught, go back to third state
                                        out=1; // out=1, we increment count
                                    end
                                else
                                    begin stt=2'b00; // go back to first state
                                        out=0;
                                    end

                                    default: stt=2'b00;

                                endcase // stt
                            end

                            always @(posedge out)
                                begin
                                    count=count+1;
                                end

                        endmodule // occur_counter

```

Test bench:

000100111000

```

// case 000100111000
module occur_counter_tb1;
    reg reset, clk;
    reg in;
    wire [2:0]count;
    wire out;

    occur_counter utt1(
        .in(in),
        .reset(reset),
        .clk(clk),
        .out(out),
        .count(count)
    )

```

```

        );

    initial begin
        clk=1;
        reset=1;
        in=1;
    end // initial

    always
        #50 clk=~clk; //10Mbps=10 Mhz= 1e-7s=> half clock =50e-9s (50 units delay)

    initial begin
        #100 reset=1'b0;
        //start the DAT 000100111000
        in=1'b0;
        #100 in=1'b0;
        #100 in=1'b0;
        #100 in=1'b1;
        #100 in=1'b0;
        #100 in=1'b0;
        #100 in=1'b1;
        #100 in=1'b1;
        #100 in=1'b1;
        #100 in=1'b0;
        #100 in=1'b0;
        #100 in=1'b0;
        #100 $finish;

    end // initial

endmodule // occur_counter_tb

```

100100100000

```

// case 100100100000
module occur_counter_tb2;
    reg reset, clk;
    reg in;
    wire [2:0]count;
    wire out;

```

```

    occur_counter utt2(
        .in(in),
        .reset(reset),
        .clk(clk),
        .out(out),
        .count(count)
    );

    initial begin
        clk=1;
        reset=1;
        in=1;
    end // initial

    always
        #50 clk=~clk;

    initial begin
        #100 reset=1'b0;
        //start the DAT 100100100000
        #100 in=1'b1;
        #100 in=1'b0;
        #100 in=1'b0;
        #100 in=1'b1;
        #100 in=1'b0;
        #100 in=1'b0;
        #100 in=1'b1;
        #100 in=1'b0;
        #100 in=1'b0;
        #100 in=1'b0;
        #100 in=1'b0;
        #100 in=1'b0;
        $finish;
    end // initial

endmodule // occur_counter_tb

```

110001101101

```
// case 110001101101
module occur_counter_tb3;
    reg reset, clk;
    reg in;
    wire [2:0]count;
    wire out;

    occur_counter utt3(
        .in(in),
        .reset(reset),
        .clk(clk),
        .out(out),
        .count(count)
    );


    initial begin
        clk=1;
        reset=1;
        in=1;
    end // initial

    always
        #50 clk=~clk;


    initial begin
        #100 reset=1'b0;
        //start the DAT 110001101101
        #100 in=1'b1;
        #100 in=1'b1;
        #100 in=1'b0;
        #100 in=1'b0;
        #100 in=1'b0;
        #100 in=1'b1;
        #100 in=1'b1;
        #100 in=1'b0;
        #100 in=1'b1;
        #100 in=1'b1;
        #100 in=1'b0;
        #100 in=1'b1;
    end
```

```
#100 $finish;
end // initial
```


000100111000

 

100100100000

 

110001101101

 

5. [10 points.]

Design a behavioral Verilog module for a 4-bit synchronous counter whose count sequence is 0, 1, 2, 3, 4,, 13, 14, 15, 14, 13, 12,, 1, 0, 1, 2,, . The output variables are *a*, *b*, *c* and *d* (*a* being the most significant bit) with *clk* as the clock variable.

Answer:

Verilog code:

```
module ctrl_4bit(a,b,c,d,clk,rst,dir); //define top entity
input clk,rst,dir; //define input signals
output a,b,c,d; //output signals
reg[3:0] ctr; //internal register
reg a,b,c,d;
initial ctr=4'b0000;

always@(posedge clk or posedge rst)
begin
    if(rst==1'b1)
        ctr<=4'b0000;
    else if (dir==1'b0) // if dir=0, it's increasing
        ctr<=ctr+4'b0001; // increment
    else if (dir==1'b1)// if dir=1, it's decreasing
        ctr<=ctr-4'b0001; // decrement

    a <= ctr[3]; //assigning counter output
    b <= ctr[2];
    c <= ctr[1];
    d <= ctr[0];
end
endmodule
```

Test bench:

```
//testbench for the 4-bit synchronous counter
module testbench();
    reg clk,rst,dir;
    wire a,b,c,d;

    ctrl_4bit uut(
        .a(a),
        .b(b),
        .c(c),
```



```
.d(d),
.clk(clk),
.rst(rst),
.dir(dir)
);

//initializing inputs
initial begin
    clk=1'b1;
    rst=1'b0;
    dir=1'b0;
    $monitor("System time(ns):",$time,"    count: %b%b%b%b",a,b,c,d);
end

//simulating inputs at various time instants
always
    #10 clk = ~clk;

always
    #300 dir=~dir;

endmodule
```

Result:

(next page)

```

# run 1000ns
System time(ns):      0      count: 0000
System time(ns):     20      count: 0001
System time(ns):     40      count: 0010
System time(ns):     60      count: 0011
System time(ns):     80      count: 0100
System time(ns):    100      count: 0101
System time(ns):    120      count: 0110
System time(ns):    140      count: 0111
System time(ns):    160      count: 1000
System time(ns):    180      count: 1001
System time(ns):    200      count: 1010
System time(ns):    220      count: 1011
System time(ns):    240      count: 1100
System time(ns):    260      count: 1101
System time(ns):    280      count: 1110
System time(ns):    300      count: 1111
System time(ns):    320      count: 1110
System time(ns):    340      count: 1101
System time(ns):    360      count: 1100
System time(ns):    380      count: 1011
System time(ns):    400      count: 1010
System time(ns):    420      count: 1001
System time(ns):    440      count: 1000
System time(ns):    460      count: 0111
System time(ns):    480      count: 0110
System time(ns):    500      count: 0101
System time(ns):    520      count: 0100
System time(ns):    540      count: 0011
System time(ns):    560      count: 0010
System time(ns):    580      count: 0001
System time(ns):    600      count: 0000
System time(ns):    620      count: 0001
System time(ns):    640      count: 0010
System time(ns):    660      count: 0011

```

