



Lab #1: Vivado

Khanh Nguyen

UIN# 525000335

ECEN 449– 503

Date: January 23, 2017

INTRODUCTION:

The purpose of the lab is to get us the first touch to get used with Vivado and Verilog. I also learned how to implement Verilog into the FPGA board (Zybo board). By using dataflow and behavioral Verilog, we were able to divide the clock rate then created a simple counter and a jackpot game.

PROCEDURE:

- 1/ An example code and constraints code for the switches was provided. I used Vivado to implement the Verilog code into the FPGA board. The LEDs should be on and off according to the switches.
- 2/ We designed a 4-bit counter that can count up or count down whenever the assigned button is pressed. The counter will have 4 inputs: UP, DOWN, RESET, and CLOCK. The output will be the LEDs on the board. I also had to create the constraints file for the according buttons and LEDs.
- 3/ The last exercise is to use the divided clock to create a jackpot game with 4 switches and 4 LEDs. I had the LEDs changing in sequential order. The player must turn on the right switch where the LED is on in order to win. I wrote the Verilog code with the constraints and debug it until it successfully implemented on hardware.

RESULT:

- 1/ I learned how to create project, create constraint and implement onto FPGA with Vivado.
- 2/ I learned how to divide the clock rate and create simple counter. I approached by dividing the clock rate since the default clock rate is 125MHz. I wanted to reduce the clock rate to 1Hz (1s/cycle) so I multiply the current clock period with 40,000,000. It resulted in 0.5s for half cycle. After 0.5s, the clock will be reversed. I used that clock for my counter to get updated every the UP, DOWN, or RESET button is pressed.
- 3/ The Jackpot game was successfully implemented onto the FPGA board. I used the same divided clock from previous exercise to get the LEDs updated. When a switch is on, a memory variable will be assigned to have the same value of that switch after 40e6 unit delays (0.5s). When the LED and the switch are the same, it will check for another condition if the memory is assigned or not. Player only wins if the switch is on and memory is **not** equal to the switch, and switch matches with LED. If the switch is on and memory is assigned, and switch doesn't match with LED, the LED will go pass the on switch.

VERILOG CODES:

counter.v

```
module counter(
input UP,
input DOWN,
input CLOCK,
input RESET,
output [3:0] LEDS
);
reg [3:0] COUNT;
reg divided_clk = 1'b0; // divided clock starts at 0
reg [31:0] counter = 1'b0; // use counter to increment the clock
always@(posedge divided_clk) //three buttons to control leds
begin
    if(RESET == 1) begin
        COUNT <= 1'b0;
    end else if (UP == 1) begin
        COUNT <= COUNT + 1; //count up
    end else if (DOWN == 1) begin
        COUNT <= COUNT - 1; //count down
    end
end
always@ ( posedge CLOCK ) //divide the clock to 1HZ (1s for one period)
begin
    counter <= counter + 1'b1;
    if ( counter == 40000000) // overtun the clk1 after 0.5s
        // clock = 125MHz=0.8E-8 (s)
        //=>(0.8E-8)*40E6=0.5s
        begin
            divided_clk <= ~divided_clk; //reverse the clock
            counter <= 1'b0; //reset the counter
        end
end
assign LEDS[3:0] = COUNT[3:0];
endmodule
```

counter.xdc

##INPUTS

```
set_property PACKAGE_PIN R18 [get_ports {UP}]
set_property IOSTANDARD LVCMOS33 [get_ports {UP}]
```

```
set_property PACKAGE_PIN P16 [get_ports {DOWN}]
set_property IOSTANDARD LVCMOS33 [get_ports {DOWN}]
```

```
set_property PACKAGE_PIN V16 [get_ports {RESET}]
set_property IOSTANDARD LVCMOS33 [get_ports {RESET}]
```

```
set_property PACKAGE_PIN L16 [get_ports {CLOCK}]
set_property IOSTANDARD LVCMOS33 [get_ports {CLOCK}]
```

##LEDS

```
set_property PACKAGE_PIN M14 [get_ports {LEDS[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LEDS[0]}]
```

```
set_property PACKAGE_PIN M15 [get_ports {LEDS[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LEDS[1]}]
```

```
set_property PACKAGE_PIN G14 [get_ports {LEDS[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LEDS[2]}]
```

```
set_property PACKAGE_PIN D18 [get_ports {LEDS[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {LEDS[3]}]
```

jackpot.v

```
module Jackpot(
input CLOCK,BUTTON,
input [3:0] SWITCHES,
input RESET,
output [3:0] LEDS
);
reg [3:0] memmory;
reg [3:0] COUNT;
reg divided_clk = 0; //clock starts at 0
reg [31:0] counter = 1'b0; // use to increment the clock
always@ ( posedge CLOCK ) //divide the clock to 1HZ
begin
    counter <= counter + 1'b1;
    if ( counter == 40000000) // overtun the clk1 after 0.5s
        // clock = 125MHz=1.25E-8 (s)
        //=>(1.25E-8)*40E6=0.5s
begin
    divided_clk <= ~divided_clk; // reverse the clock
    counter <= 1'b0;// reset clock
```

```

        end
    end
always@(posedge divided_clk)
    begin
        if ( RESET ) //reset the LEDS
            begin
                COUNT = 4'b1000;
            end
        else if ( COUNT == 4'b0001 ) //let the LEDS glowing in cycle
            begin
                COUNT = 4'b1000;
            end
        else if (SWITCHES)
            begin
                #40000000 memmory<=SWITCHES; // save the position of the switch after 0.5s
                if ( (COUNT == SWITCHES) && (SWITCHES!=memmory) ) //detect the switch, if
memmory== switch it doesnt work
                    begin
                        COUNT = 4'b1111; //win the jackpot
                    end
                else
                    begin
                        COUNT = {COUNT[0], COUNT[3:1]};
                    end
            end
        end
    else
        begin
            COUNT = {COUNT[0], COUNT[3:1]}; //move the 1 in cycle,keep the LEDS
glowing sequentially
        end
    end
    assign LEDS[3:0] = COUNT[3:0]; //assign COUNT to LEDS
endmodule

```

jackpot.xdc

##SWITCHES INPUTS

```

set_property PACKAGE_PIN G15 [get_ports {SWITCHES[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {SWITCHES[0]}]

```

```
set_property PACKAGE_PIN P15 [get_ports {SWITCHES[1]}]
set_property IOSTANDARD LVC MOS33 [get_ports {SWITCHES[1]}]
```

```
set_property PACKAGE_PIN W13 [get_ports {SWITCHES[2]}]
set_property IOSTANDARD LVC MOS33 [get_ports {SWITCHES[2]}]
```

```
set_property PACKAGE_PIN T16 [get_ports {SWITCHES[3]}]
set_property IOSTANDARD LVC MOS33 [get_ports {SWITCHES[3]}]
```

```
set_property PACKAGE_PIN L16 [get_ports {CLOCK}]
set_property IOSTANDARD LVC MOS33 [get_ports {CLOCK}]
```

##LEDs OUTPUTS

```
set_property PACKAGE_PIN M14 [get_ports {LEDS[0]}]
set_property IOSTANDARD LVC MOS33 [get_ports {LEDS[0]}]
```

```
set_property PACKAGE_PIN M15 [get_ports {LEDS[1]}]
set_property IOSTANDARD LVC MOS33 [get_ports {LEDS[1]}]
```

```
set_property PACKAGE_PIN G14 [get_ports {LEDS[2]}]
set_property IOSTANDARD LVC MOS33 [get_ports {LEDS[2]}]
```

```
set_property PACKAGE_PIN D18 [get_ports {LEDS[3]}]
set_property IOSTANDARD LVC MOS33 [get_ports {LEDS[3]}]
```

```
set_property PACKAGE_PIN R18 [get_ports {RESET}]
set_property IOSTANDARD LVC MOS33 [get_ports {RESET}]
```

QUESTIONS:

1/The use push buttons are connected like below:

BTN[0]=R18 (up button in counter and reset button in jackpot)

BTN[1]=P16 (down button in counter)

BTN[2]=V16 (reset button in jackpot)

BTN[3]=Y16

2/ The purpose of an edge detection circuit is to know when a signal gets updated. Therefore, all the components can be implemented synchronously. In this lab, it is used as a clock to have the LEDs to be on every equal clock cycle.